

# Digital System Design Lab Report, Lab4

Author: Ying Yiwen  
Number: 12210159

## Abstract

## Contents

<b>1</b>	<b>Introduction</b>	<b>2</b>
<b>2</b>	<b>Sequential Signal Generator</b>	<b>2</b>
2.1	VHDL Code . . . . .	2
2.2	Testbench Code . . . . .	3
2.3	Therotical Analysis . . . . .	4
2.4	Simulation Result . . . . .	4
<b>3</b>	<b>Sequential Signal Detector</b>	<b>4</b>
3.1	VHDL Code . . . . .	4
3.2	Testbench Code . . . . .	5
3.3	Therotical Analysis . . . . .	7
3.4	Simulation Result . . . . .	7
<b>4</b>	<b>Conclusion</b>	<b>7</b>

# 1 Introduction

## 2 Sequential Signal Generator

### 2.1 VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity sequence_generator is
    Port (
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        dataout : out STD_LOGIC
    );
end sequence_generator;

architecture Behavioral of sequence_generator is
    signal current_state : std_logic_vector (2 downto 0) := (others => '0');
    signal next_state : std_logic_vector (2 downto 0) := (others => '0');
begin
    -- accident
    process (clk, reset) is
    begin
        if reset = '1' then
            current_state <= "000";
        elsif clk'event and clk = '1' then
            current_state <= next_state;
        end if;
    end process;

    -- state transfer
    process (current_state) is
    begin
        case current_state is
            when "000" =>
                dataout <= '1';
                next_state <= "001";
            when "001" =>
                dataout <= '1';
                next_state <= "010";
            when "010" =>
                dataout <= '0';
                next_state <= "011";
            when "011" =>
                dataout <= '1';
                next_state <= "100";
            when "100" =>
                dataout <= '1';
                next_state <= "101";
            when "101" =>
                dataout <= '1';
                next_state <= "110";
            when "110" =>
```

```

        dataout <= '0';
        next_state <= "000";
    when others =>
        dataout <= '0';
        next_state <= "000";
    end case;
end process;
end Behavioral;

```

## 2.2 Testbench Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity testbench is
end testbench;

architecture tb of testbench is
component sequence_generator is
    Port (
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        dataout : out STD_LOGIC
    );
end component;

signal clk : STD_LOGIC := '0';
signal reset : STD_LOGIC := '0';
signal dataout : STD_LOGIC;
constant period : time := 10 ns;

begin
    uut: sequence_generator port map (
        clk => clk,
        reset => reset,
        dataout => dataout
    );

    clk <= not clk after period / 2;


    tb: process is
    begin
        reset <= '1';
        wait for period;
        reset <= '0';
        wait for period;
        wait;
    end process;

end tb;


```

## 2.3 Therotical Analysis


## 2.4 Simulation Result

 

(a) Behavioral Simulation Result

 


(b) Post-Synthesis Simulation Result

 


(c) Post-Implementation Simulation Result

Figure 1: Simulation Result

 

(a) Behavior Schematic

 

(b) Behavior Schematic

Figure 2: Schematic Result

## 3 Sequential Signal Detector

### 3.1 VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity sequence_generator is
    Port (
        clk : in STD_LOGIC;

```

```

        reset : in STD_LOGIC;
        input  : in STD_LOGIC;
        dataout : out STD_LOGIC
    );
end sequence_generator;

architecture Behavioral of sequence_generator is
    signal current_state : std_logic_vector(1 downto 0) := "00";
    signal next_state : std_logic_vector(1 downto 0);
begin
    process(clk, reset)
    begin
        if reset = '1' then
            current_state <= "00";
        elsif CLK'event and CLK = '1' then
            current_state <= next_state;
        end if;
    end process;

    -- next state logic
    with current_state & input select
        next_state <=
            "00" when "000",
            "01" when "001",
            "10" when "010",
            "01" when "011",
            "00" when "100",
            "11" when "101",
            "11" when "110",
            "11" when "111",
            "00" when others;

    with current_state & input select
        dataout <=
            '0' when "000" | "001" | "010" | "011" | "100",
            '1' when "101" | "110" | "111",
            '0' when others;

end Behavioral;

```

## 3.2 Testbench Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity testbench is
end testbench;

architecture tb of testbench is
    component sequence_generator is
        Port (
            clk : in STD_LOGIC;
            reset : in STD_LOGIC;

```

```

    input : in STD_LOGIC;
    dataout : out STD_LOGIC
);
end component;

signal clk : STD_LOGIC := '0';
signal reset : STD_LOGIC := '0';
signal input : STD_LOGIC;
signal dataout : STD_LOGIC;
constant period : time := 10 ns;

begin
    uut: sequence_generator port map (
        clk => clk,
        reset => reset,
        input => input,
        dataout => dataout
    );

    clk <= not clk after period / 2;

    tb: process is
    begin
        for i in 1 to 10 loop
            reset <= '1';
            wait for period;
            reset <= '0';
            wait for period;


            for j in 1 to 2 loop
                input <= '0';
                wait for period;
                input <= '1';
                wait for period;
                input <= '1';
                wait for period;
                input <= '1';
                wait for period;
                input <= '0';
                wait for period;
                input <= '1';
                wait for period;
                input <= '1';
                wait for period;
            end loop;
        end loop;
        wait;
    end process;

end tb;


```

### 3.3 Therotical Analysis


### 3.4 Simulation Result

 

(a) Behavioral Simulation Result

 


(b) Post-Synthesis Simulation Result

 


(c) Post-Implementation Simulation Result

Figure 3: Simulation Result

 

(a) Behavior Schematic

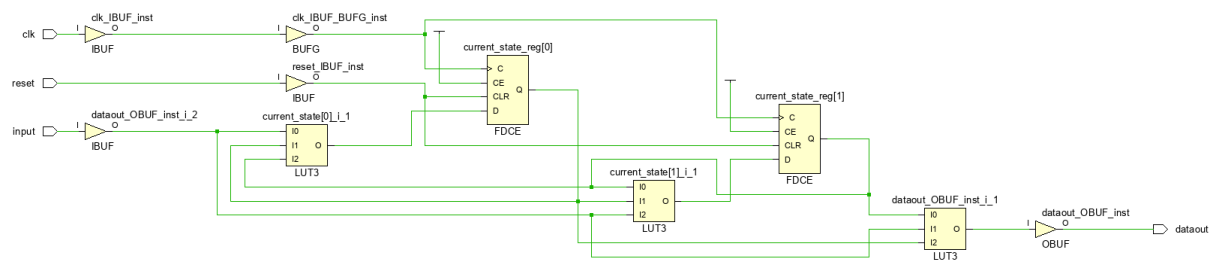

(b) Behavior Schematic

Figure 4: Schematic Result

## 4 Conclusion